


Leonardo Mattos Martins

U25267206

Lab 6 Writeup

Lab Tasks

1. Simulate the Basic CPU

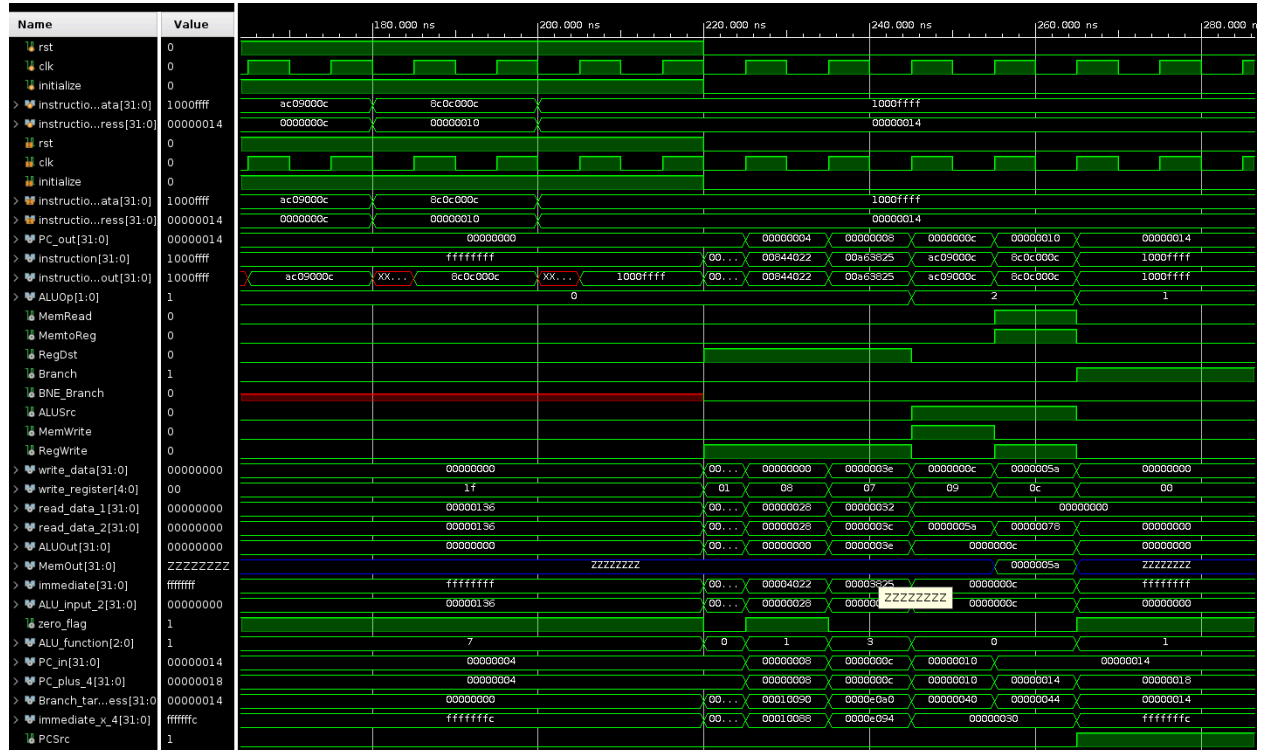

The CPU has reset portion for 220 ns before executing the instructions provided in the tb_cpu.v testbench. This CPU is implemented in a single-cycled way, where no pipeline registers delay the execution of an instruction for longer than one clock cycle.

2. SLT


Instructions:

ADD R1,R0,R2

ADD R1,R0,R2

SLT R3,R1,R2

SLT R3,R2,R1

 


Modifications:

ALU_Control.v - added the slt instruction (func = 3'd5)

ALU.v - added slt function (a<b)?1:0

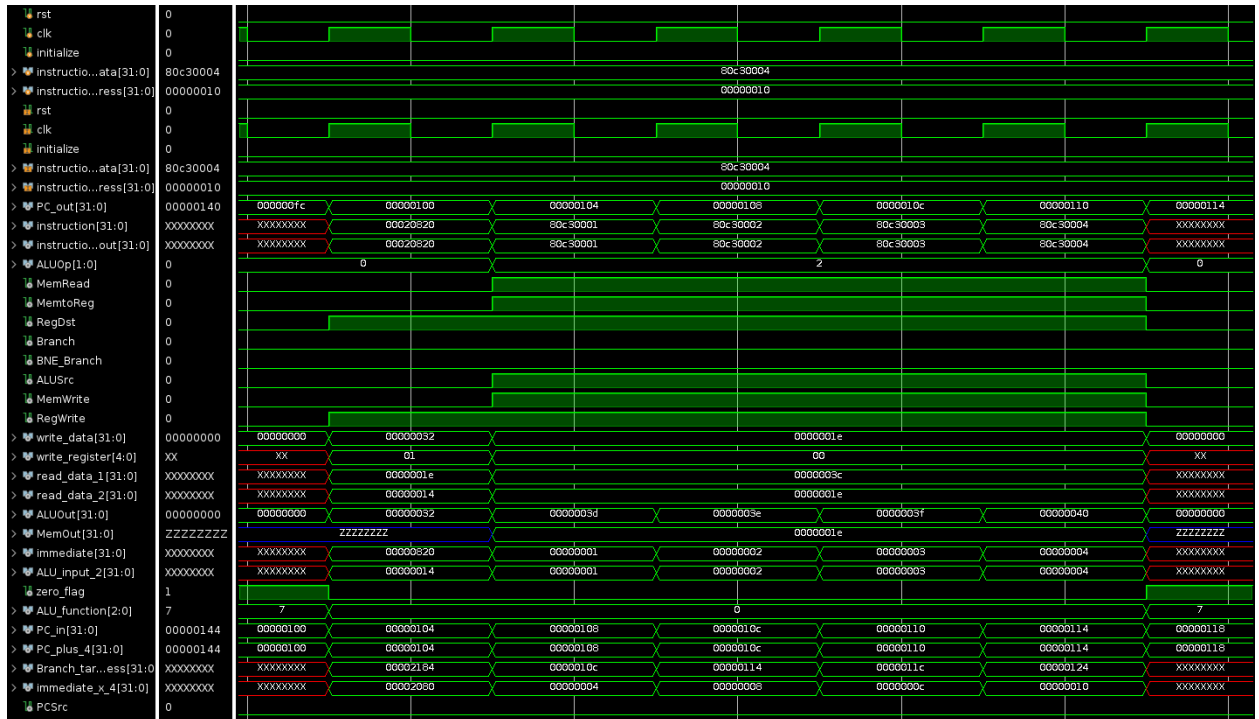3. ADDI

```
ADD R1,R0,R2
ADDI R3,R2,1
ADDI R3,R2,2
ADDI R3,R2,3
ADDI R3,R2,4
```



Modifications:


control.v - added ADDI instruction with required opcode and the following settings (ALUOp = 2'b10; MemRead = 1'b1; MemtoReg = 1'b1; RegDst = 1'b1; Branch = 1'b0; ALUSrc = 1'b1; MemWrite = 1'b1; RegWrite = 1'b1; BNE_Branch = 1'b0;)

4. J

ADD R2,R0,R2

ADD R2,R0,R2

J -3

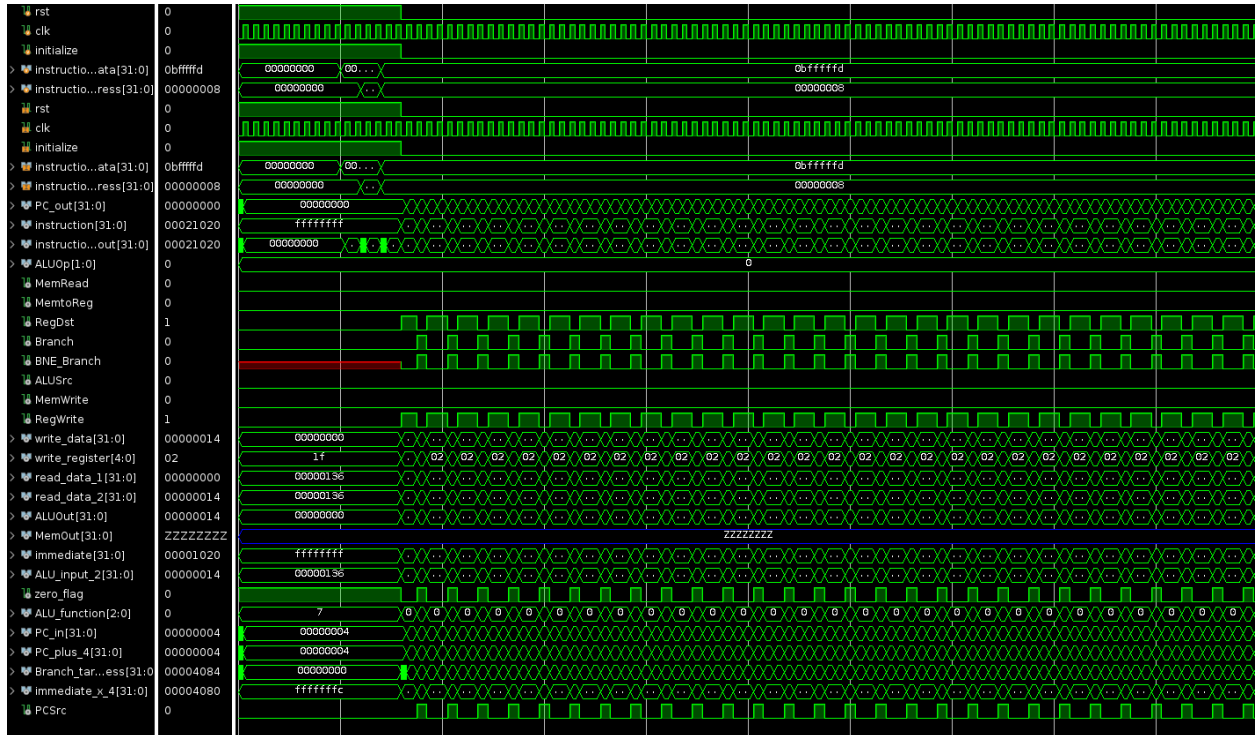

Modifications:

cpu.v - Added a BNE_Branch control signal for both BNE and J instructions. For a J instruction, both BEQ and BNE_Branch signals are enabled such that it will jump regardless of BEQ or BNE.

control.v - Added the BNE_Branch control signal to each of the other options in control, and added J instruction with the following settings (ALUOp = 2'b00; MemRead = 1'b0; MemtoReg = 1'b0; RegDst = 1'b0; Branch = 1'b1; ALUSrc = 1'b0; MemWrite = 1'b0; RegWrite = 1'b0;)


5. BNE

```
ADD R1,R0,R2
```

```
ADD R1,R0,R2
```

```
BNE R1,R1,-3
```

```
BNE R1,R2,-4
```

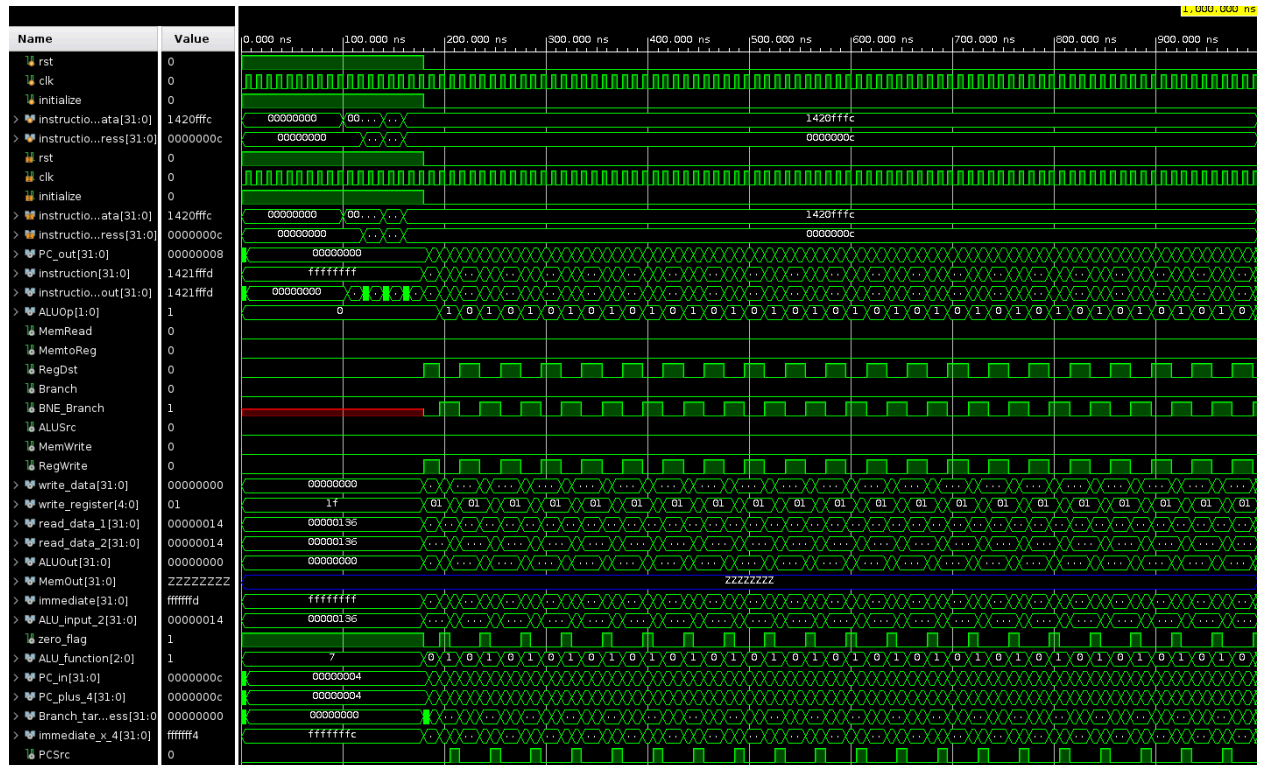

Modifications:

cpu.v - Added a BNE_Branch control signal and additional logic to branch if Branch and the zero_flag is on or if BNE_Branch and not zero_flag is on.

control.v - Added BNE instruction with the following settings (ALUOp = 2'b01; MemRead = 1'b0; MemtoReg = 1'b0; RegDst = 1'b0; Branch = 1'b0; ALUSrc = 1'b0; MemWrite = 1'b0; RegWrite = 1'b0; BNE_Branch = 1'b1)

